

FRIDA PCB Analog Front-End

February 17, 2026

Constraints

- ▶ Sampling-rate target: 10 MS/s nominal, up to 50 MS/s.
- ▶ ADC analog rails: 0 V to 1.2 V.
- ▶ Required output common-mode range: 0.1 V to 1.1 V.
- ▶ Required differential output range: -1.2 V to +1.2 V (2.4 V total).
- ▶ 50 Ω source, 80 MHz generator: 33250A Keysight
- ▶ ADC input assumption: $R_{in} \approx 2 \text{ k}\Omega$, $C_{in,single} \approx 2 \text{ pF}$.
- ▶ ADC quantization noise reference: $(1.2 \text{ V}/2^{12})/\sqrt{12}$.
- ▶ Amplifier noise target: $< 20\%$ of ADC quantization noise.

Selected Driver: THS4541

- ▶ Fully differential amplifier for SE-to-diff conversion and ADC drive.
- ▶ Nominal BW class: 850 MHz (datasheet), with >500 MHz at gain of 2.
- ▶ Input voltage noise density: $2.2 \text{ nV}/\sqrt{\text{Hz}}$ ($f > 100 \text{ kHz}$).
- ▶ Output linear swing headroom: about 0.2 V from each rail.
- ▶ V_{OCM} loop range (approx):

$$V_{S-} + 0.91 \text{ V} \leq V_{\text{OCM}} \leq V_{S+} - 1.1 \text{ V}$$

- ▶ Datasheet: [TI THS4541](#)
- ▶ App note: [SNOA461A](#)

Nyquist LPF Driver Requirements

Amplifier Specification	Requirement
Bandwidth (0.1 dB)	$\approx f_s/2$
H2 and H3	$\approx 20 \log_{10}(1/2^N)$
Balance error	$\approx \text{ADC LSB at } f_s/2$
Settling time	$\approx 0.5 \cdot (1/f_s)$
Noise	$\approx \text{ADC floor, with amp 6 dB lower}$

Chosen Architecture and Equations

- ▶ Architecture: THS4541 differential driver + output RC anti-alias stage.
- ▶ Matched FDA differential gain:

$$A_{vd} \approx \frac{R_F}{R_G}$$

- ▶ Unity differential gain target: $R_F = R_G$ on both sides.
- ▶ First-order cutoff with differential capacitor across ADC inputs:

$$f_c \approx \frac{1}{2\pi(2R_O)(C_O + C_{in,diff})}$$

- ▶ Per-side shunt form:

$$f_c \approx \frac{1}{2\pi R_O(C_{O,side} + C_{in,single})}$$

Calculated Values: Gain and Interface

- ▶ Max sampling rate: $f_s = 50 \text{ MS/s}$.
- ▶ Target anti-alias pole: $f_c \approx 25 \text{ MHz}$.
- ▶ Unity-gain FDA: $R_F = R_G = 499 \text{ } \Omega$ (both sides).
- ▶ Input-shunt terminations are **R14** and **R15** (both $54.9 \text{ } \Omega$), used as R_T .
- ▶ FDA gain network in this schematic: **R18/R19** as $R_G = 499 \text{ } \Omega$ and **R22/R23** as $R_F = 499 \text{ } \Omega$.
- ▶ First-order static estimate per input:

$$Z_{in} \approx R_T \parallel R_G \approx 54.9 \parallel 499 \approx 49.5 \text{ } \Omega$$

For a tighter 50- Ω static match, set R_T near **54.9** Ω .

Calculated Values: Output Filter

- ▶ Method reference: [AN-1393 \(SNOA461A\)](#).
- ▶ Output isolation/filter resistors: **R24, R25**; target $R_O = 56\ \Omega$ per side.
- ▶ $56\ \Omega$ is for ADC kickback isolation/stability, not $50\text{-}\Omega$ source matching.
- ▶ Per-side solve ($f_c = 25\text{ MHz}$, $C_{in,single} = 2\text{ pF}$): $C_{O,side} = \frac{1}{2\pi R_O f_c} - C_{in,single} \approx 111.7\text{ pF}$.
Use **110 pF** per side $\Rightarrow f_c \approx 25.4\text{ MHz}$.
- ▶ Differential solve: $C_{O,diff} = \frac{1}{2\pi(2R_O)f_c} - C_{in,diff} \approx 52.8\text{ pF}$. Use **51 pF** across $OUT+/OUT-$
 $\Rightarrow f_c \approx 25.7\text{ MHz}$.

100-Ω Differential Pair from Stackup

From the shown stackup (TOP over IN2 reference plane):

$$h = 140 \mu\text{m}, \quad \varepsilon_r = 4.00, \quad t = 35 \mu\text{m}$$

Core values from the image: $1200 \mu\text{m}$, $\varepsilon_r = 4.60$.

Single-ended microstrip estimate:


$$Z_0 \approx \frac{87}{\sqrt{\varepsilon_r + 1.41}} \ln \left(\frac{5.98h}{0.8W + t} \right)$$

Edge-coupled differential approximation:

$$Z_{\text{diff}} \approx 2Z_0 \left(1 - 0.48e^{-0.96S/h} \right)$$

Use $W = 180 \mu\text{m}$ and $S = 200 \mu\text{m}$. With this stackup, the first-pass estimate is:
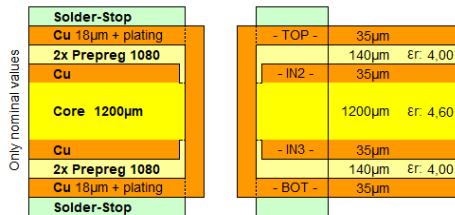
$$Z_0 \approx 58 \Omega, \quad Z_{\text{diff}} \approx 101 \Omega$$



Source: from Multicb